

Joseph Godinez

Computer Science 240-20


Professor Oscar Ho

September 22, 2021

### Problem set


1. If C,D,E are 1 and A,B,F are negated then the output will be 1

A	B	C	Out
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

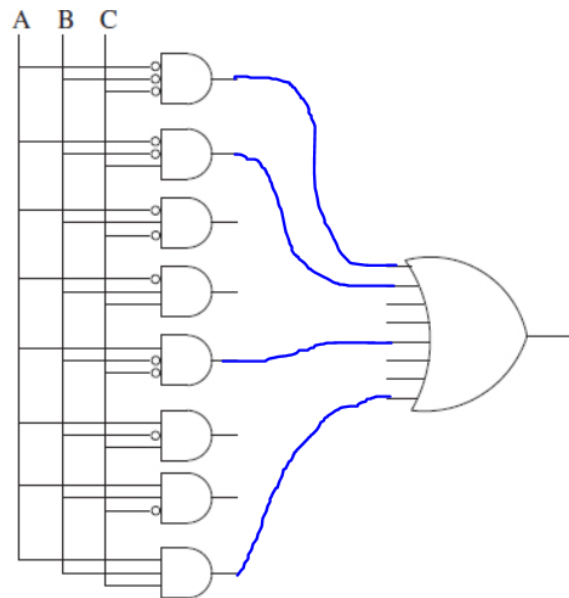

2.

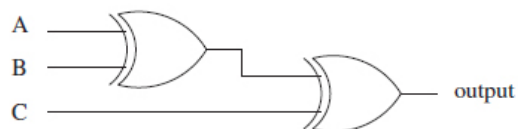**3.14** The following logic circuits consist of two exclusive-OR gates. Construct the output truth table.



A	B	C	output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

3.

**3.16** Fill in the truth table for a two-input NOR gate.


A	B	A NOR B
0	0	1
0	1	0
1	0	0
1	1	0

4.

5. A five input decoder would probably have about thirty two because  $2^5$ .

6. A sixteen multiplexer has only one output line, but will have four select lines.

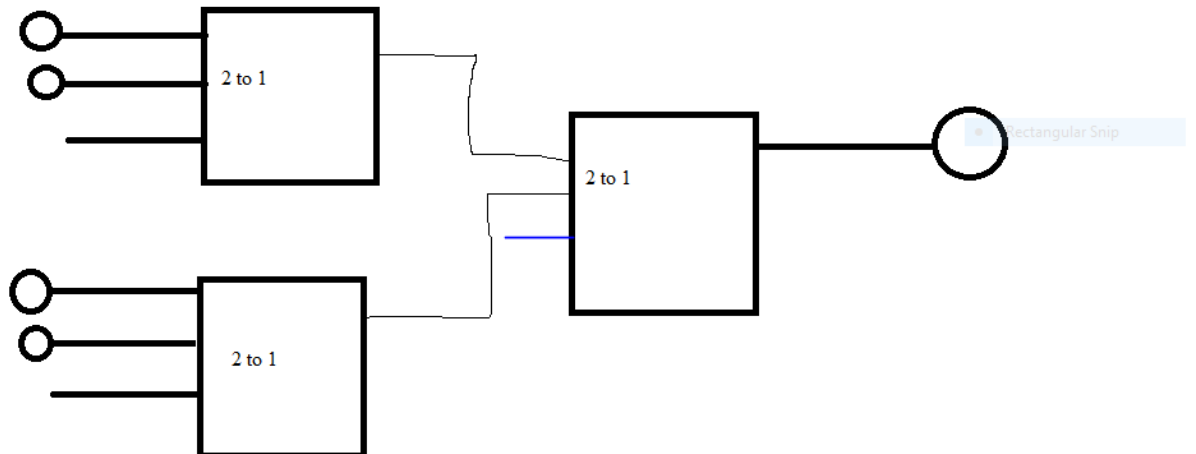
7. The number of nibbles in a memory are 32768 because it is  $2^{14} = 16384$  then you multiply that by 2 to get 32768.



8.

**3.29** Given the logic circuit in Figure 3.41, fill in the truth table for the output value Z.

A	B	C	Z
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

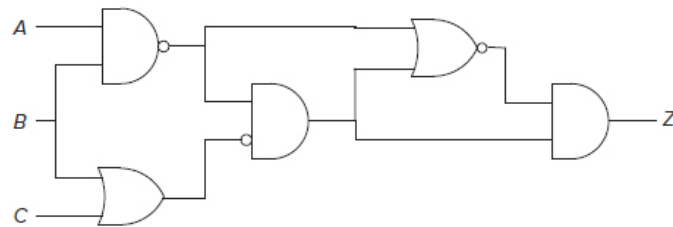

**Figure 3.41** Diagram for Exercise 3.29.

9.

10. The number of storage that the memory contain is about 12582912 because the address bit is 22 while the bit entry is 3 so  $2^{22} * 3$ .